

# Circuits

## 9.1 Power

The power is the energy dissipated (or work done  $W$ ) per unit time. The electrical power produced by an electric current  $I$  consisting of a charge  $Q$  passing through an electrical potential  $V$  every  $t$  seconds is

$$P = \frac{W}{t} = \frac{W Q}{Q t} = IV. \quad (9.1)$$

In order to introduce geometry to circuit problems, we typically resort to the resistivity of the circuit, which is geometry-dependent. The resistivity  $\rho$  of a wire of cross-sectional area  $A$ , length  $\ell$  and resistance  $R$  is

$$\rho = \frac{RA}{\ell} \quad (9.2)$$

i.e., the resistance of the wire is inversely proportional to its cross-sectional area, i.e., the resistance is also dependent upon the geometry. A smaller area gives rise to a larger resistance.

In the case of resistive loads, we can substitute Ohm's law  $V = IR$  into equation (9.1) to give

$$P = I^2 R. \quad (9.3)$$

When discussing resistive circuits using equation (9.3), this power is strictly the power dissipated by a resistor of resistance  $R$  when a current  $I$  is flowing through it—this power strictly concerns energy which is converted from electrical to thermal energy, over some time  $t$ . Equation (9.3) is also idealised, and assumes that all electrical energy is turned into heat. This effect is known as Joule heating.

## 9.2 Internal resistance

The internal resistance  $r$  is a small (but sometimes non-negligible) amount of resistance inside cells and batteries, opposing the flow of current. Internal resistance is a source of heat loss in a circuit.

The terminal potential difference across the circuit (i.e., the input voltage) is thus dependent upon the electromotive force  $\mathcal{E}$  of the battery and the potential difference across the resistor  $Ir$ , i.e.,

$$V = \mathcal{E} - Ir. \quad (9.4)$$

A smaller internal resistance  $r$  means that the battery can supply more current for the same  $V - \mathcal{E}$ . Internal resistance is an important design consideration in engineering applications.

Which terminal p.d. and internal resistance does the national grid require?

a) low terminal p.d., low $r$	b) low terminal p.d., high $r$
c) high terminal p.d., low $r$	d) high terminal p.d., high $r$